

# ModelSim Tutorial for EECS361

*Fall 2014*

*Kaicheng Zhang(kaichengz@u.northwestern.edu)*

## Introduction

This tutorial will build a 1-bit full adder and a SRAM reader in VHDL. It uses ModelSim as the compiler and the simulator. The purpose of this tutorial has two folds:

- 1) Give an example on how to create a new project, write VHDL codes, compile the project and do simulations in ModelSim.
- 2) Give an example on how to utilize the component provided by the course library.

## 1-bit Full Adder

### Start ModelSim

1. Login to one of the linux machines in Wilkinson Lab.
2. Open the terminal.
3. type the following command:


```
source /vol/ece303/ece303.env
```

4. Start ModelSim by typing:


```
vsim
```

### Create a new project

1. Select File -> New -> Project...

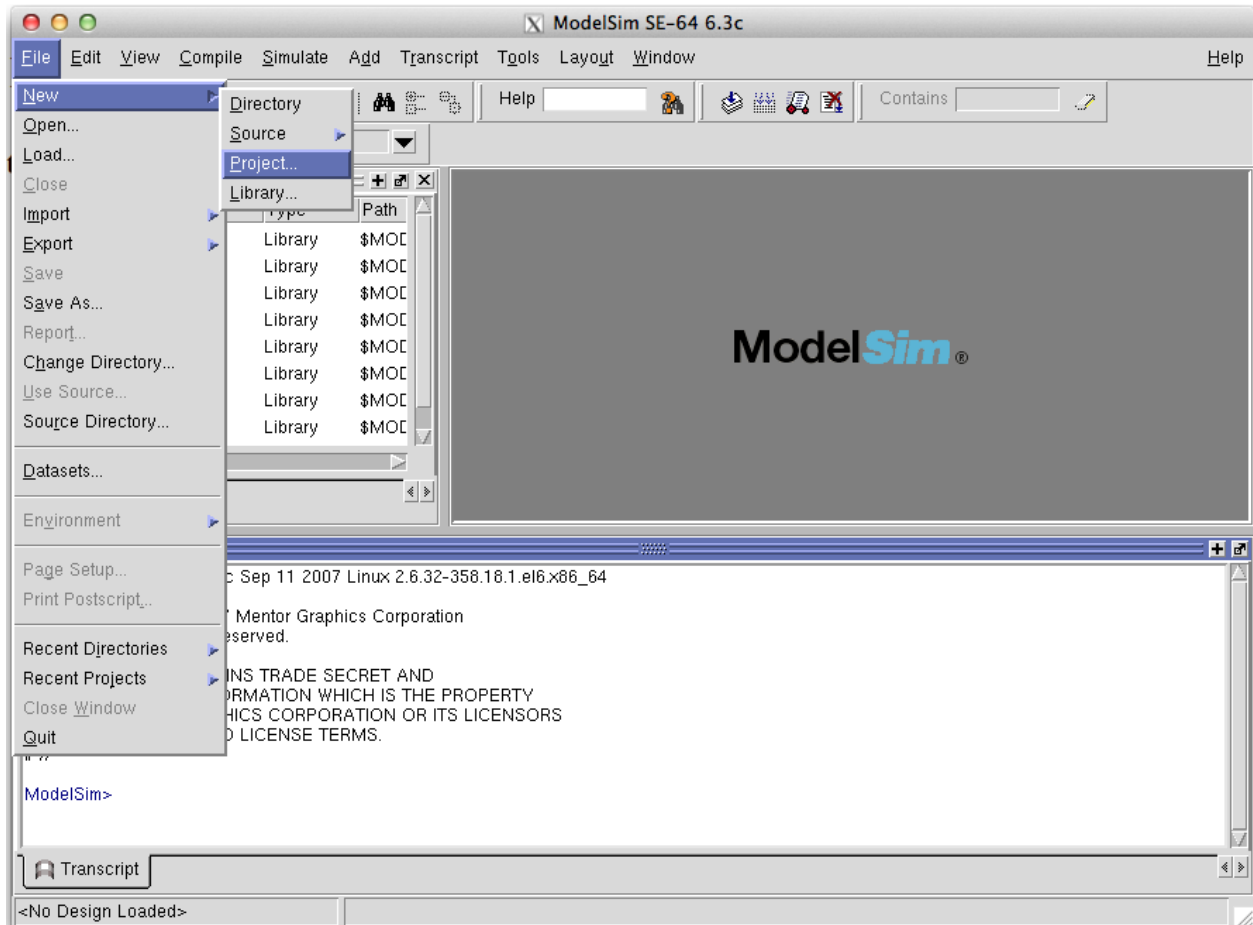

 2. Fill in the “Project Name” and “Project Location”. The “Project Location” is where you want to put your project in. Leave the other fields unchanged. Click OK. If a new dialogue pops out asking you to create the directory, click OK.



3. ModelSim will ask you to add items to the project right after your project is created. You can do

it now or do it later. In this tutorial, we simply close this dialogue.


## **Add EECS 361 library files to the project**

We have a number of gates and other components ready for you to use.


1. Copy all the files in “lib” directory of the library package to your own project’s directory. Here is the full list of the files:

and\_gate\_32.vhd  
and\_gate\_n.vhd  
and\_gate.vhd  
dec\_n.vhd  
dffr.vhd  
dff.vhd  
eecs361\_gates.vhd  
eecs361.vhd  
mux\_32.vhd  
mux\_n.vhd  
mux.vhd  
nand\_gate\_32.vhd  
nand\_gate\_n.vhd  
nand\_gate.vhd  
nor\_gate\_32.vhd  
nor\_gate\_n.vhd  
nor\_gate.vhd  
not\_gate\_32.vhd  
not\_gate\_n.vhd  
not\_gate.vhd  
or\_gate\_32.vhd  
or\_gate\_n.vhd  
or\_gate.vhd  
sram.vhd  
syncram.vhd  
xnor\_gate\_32.vhd  
xnor\_gate\_n.vhd  
xnor\_gate.vhd  
xor\_gate\_32.vhd  
xor\_gate\_n.vhd  
xor\_gate.vhd

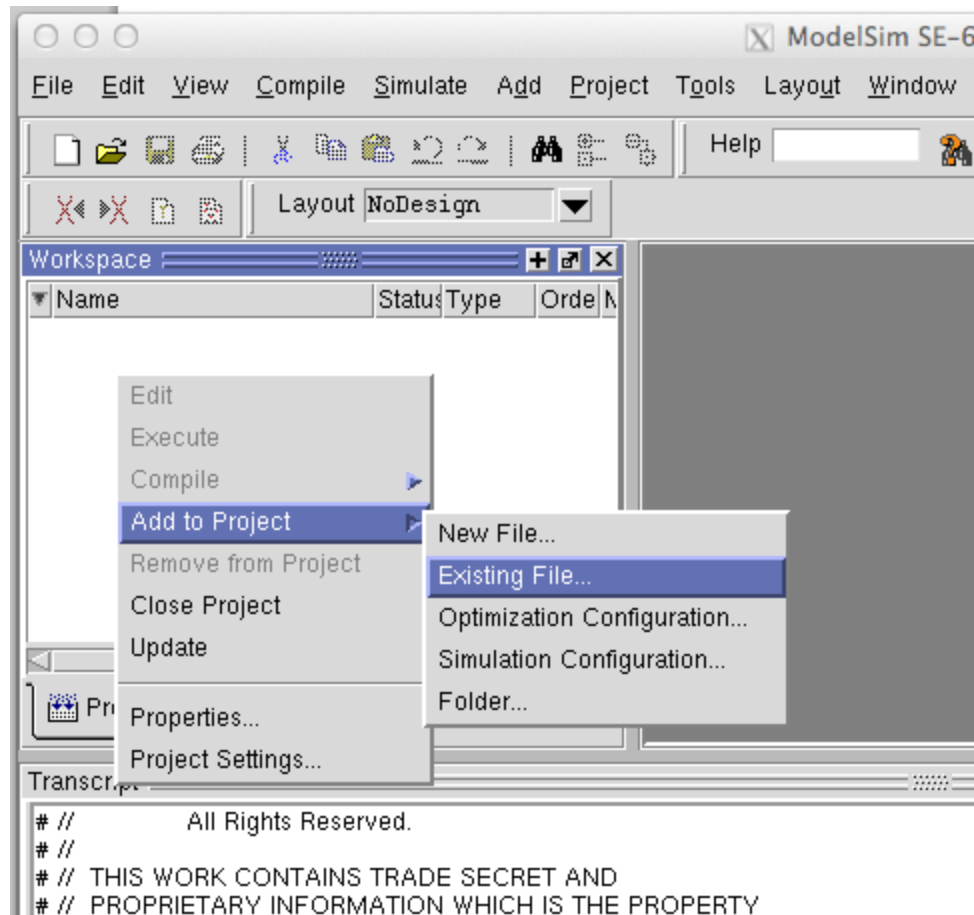
2. In the Workspace window, right click, select “Add to Project” -> “Existing File...”.



 
2. Click on “Browse...” to open the file selection window.



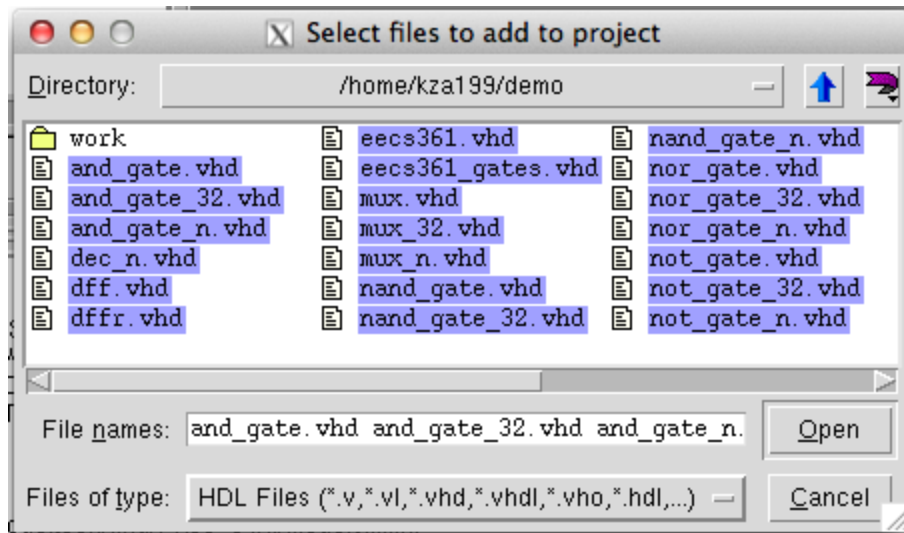3. The window should start at your project’s location by default. If not, navigate yourself to your project’s location. Use Ctrl and Shift keys to select all the vhd files. Click on Open, and then click on OK.



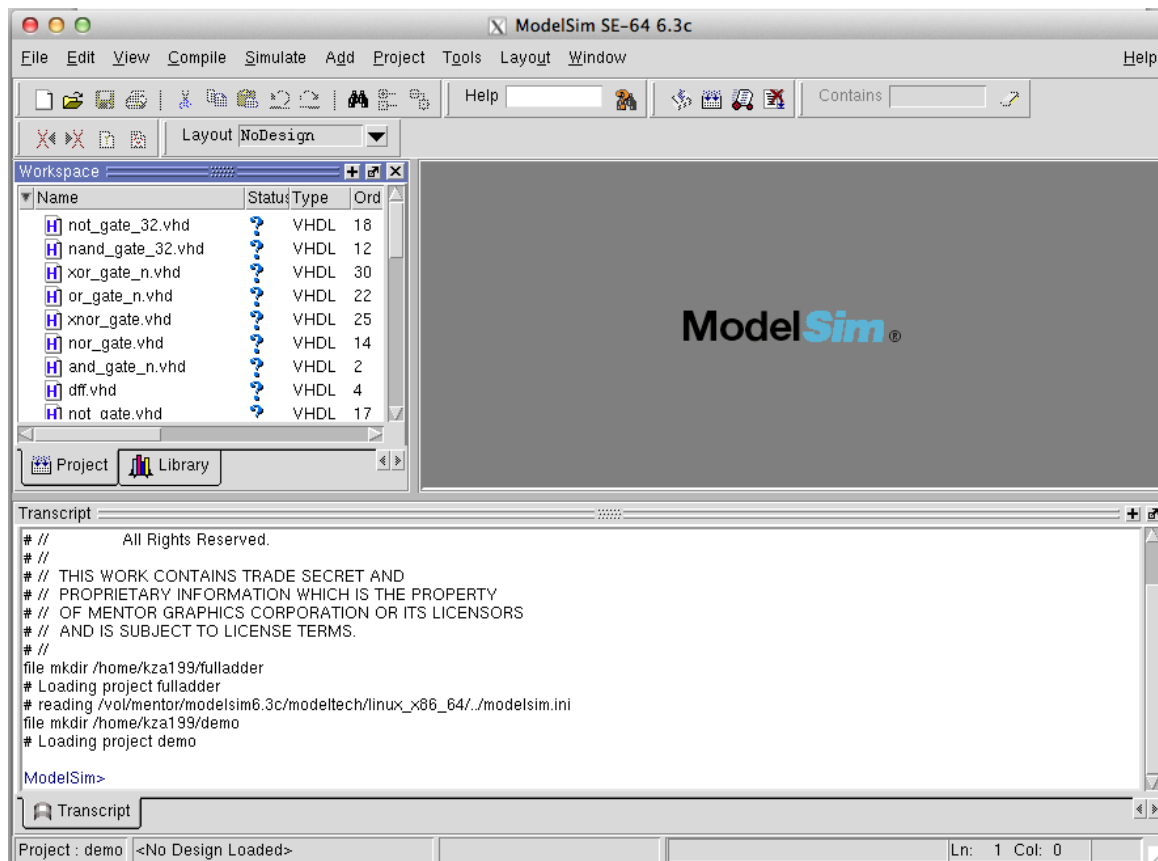4. You should return to the main window, with the vhd files added to your workspace. Feel free to double click on the file names to check what in the fil



## Create the 1-bit full adder

1. Select File -> New -> Source -> VHDL to create a new VHDL source file.
2. Write the fulladder VHDL code:

```

library ieee;
use ieee.std_logic_1164.all;
use work.eecs361_gates.all;

entity fulladder is
  port (
    x      : in  std_logic;
    y      : in  std_logic;
    c      : in  std_logic;
    z      : out std_logic;
    cout   : out std_logic
  );
end fulladder;

architecture structural of fulladder is
  signal xor0 : std_logic;
  signal and0 : std_logic;
  signal and1 : std_logic;
begin
  xor0_map : xor_gate port map (x => x, y => y, z => xor0);
  xor1_map : xor_gate port map (x => xor0, y => c, z => z);
  and0_map : and_gate port map (x => x, y => y, z => and0);
  and1_map : and_gate port map (x => xor0, y => c, z => and1);
  or0_map  : or_gate port map (x => and0, y => and1, z => cout);
end architecture structural;

```

3. Save the file as fulladder.vhd

4. Add fulladder.vhd to your workspace.

### Create testbench for fulladder.

1. As the steps above, create another VHDL file “fulladder\_demo.vhd”, write the following content, and add it to the workspace.

```

library ieee;
use ieee.std_logic_1164.all;

entity fulladder_demo is
  port (
    z      : out std_logic;
    cout   : out std_logic
  );
end fulladder_demo;

architecture structural of fulladder_demo is

```



```

component fulladder is
  port (
    x      : in  std_logic;
    y      : in  std_logic;
    c      : in  std_logic;
    z      : out std_logic;
    cout   : out std_logic
  );
end component fulladder;
signal xin : std_logic;
signal yin : std_logic;
signal cin : std_logic;
signal inbus : std_logic_vector(2 downto 0);
begin
  fulladder_map : fulladder port map (x => xin, y => yin, c => cin, z
=> z, cout => cout);
  cin <= inbus(2);
  yin <= inbus(1);
  xin <= inbus(0);


  test_proc : process
  begin
    inbus <= "000";
    wait for 5 ns;
    inbus <= "001";
    wait for 5 ns;
    inbus <= "010";
    wait for 5 ns;
    inbus <= "011";
    wait for 5 ns;
    inbus <= "100";
    wait for 5 ns;
    inbus <= "101";
    wait for 5 ns;
    inbus <= "110";
    wait for 5 ns;
    inbus <= "111";
    wait for 5 ns;
    wait;
  end process;
end architecture structural;

```

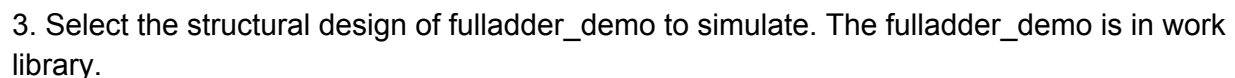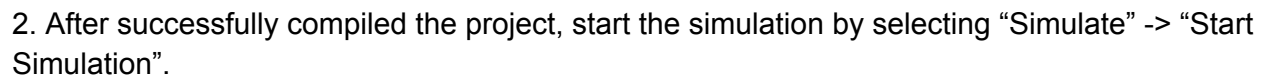
1. Compile all the files by selecting Compile -> "Compile All". Try a second time or third time if the first compilation generates errors. Because the default order of the files may not match the dependencies between components.



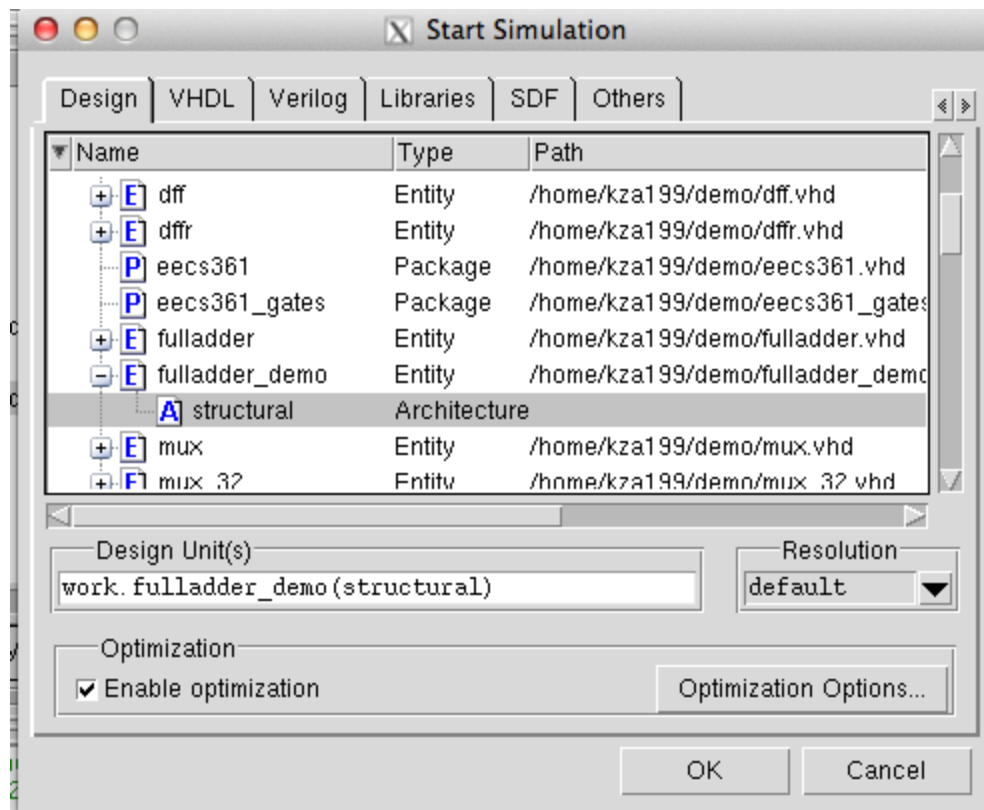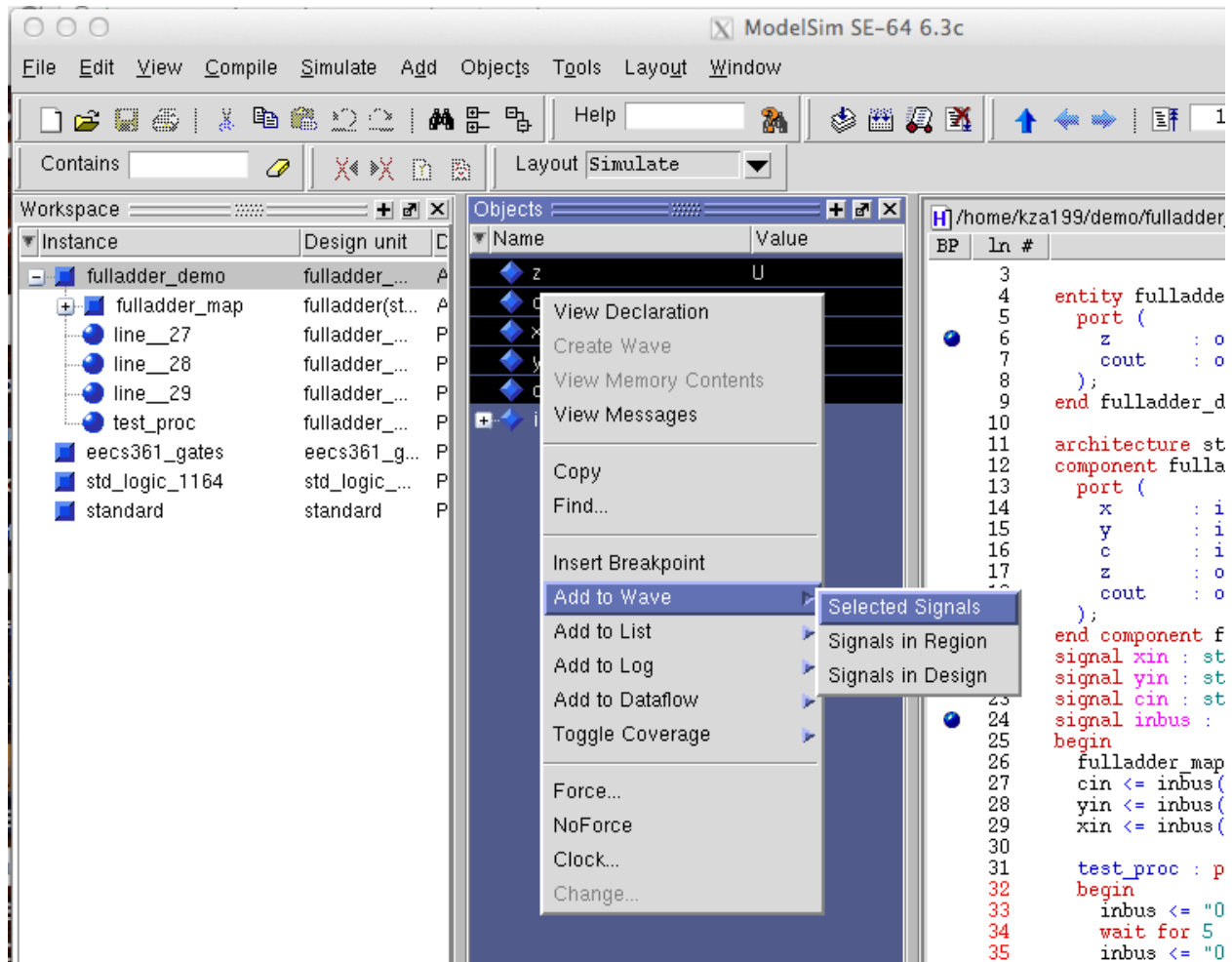
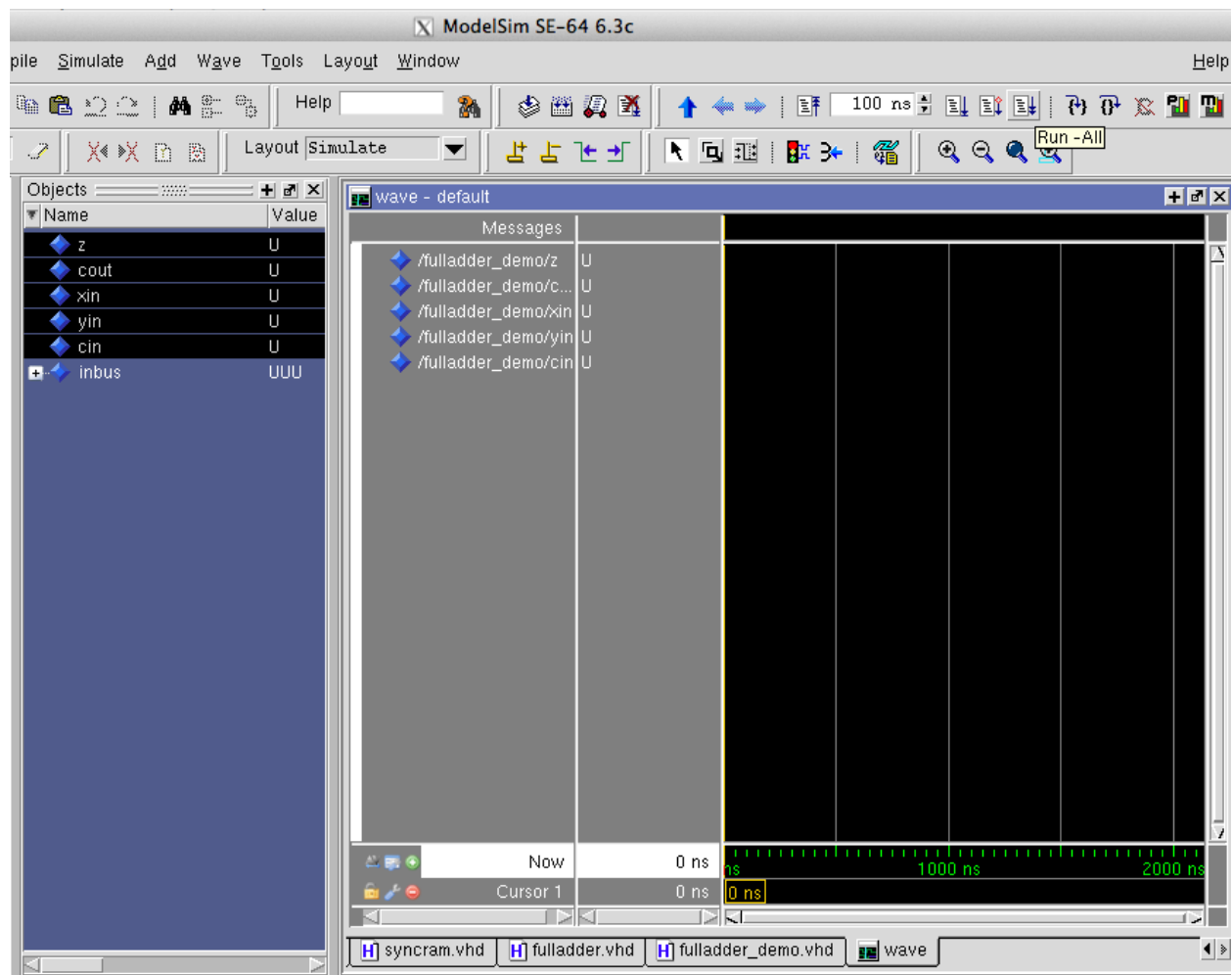





4. A simulation window will pop out. In the Objects window in the middle, select z, cout, xin, yin, and cin. After that, right click on them, then select "Add to Wave" -> "Selected Signals".



5. A wave window will appear in the right. Click “Run -All” button .



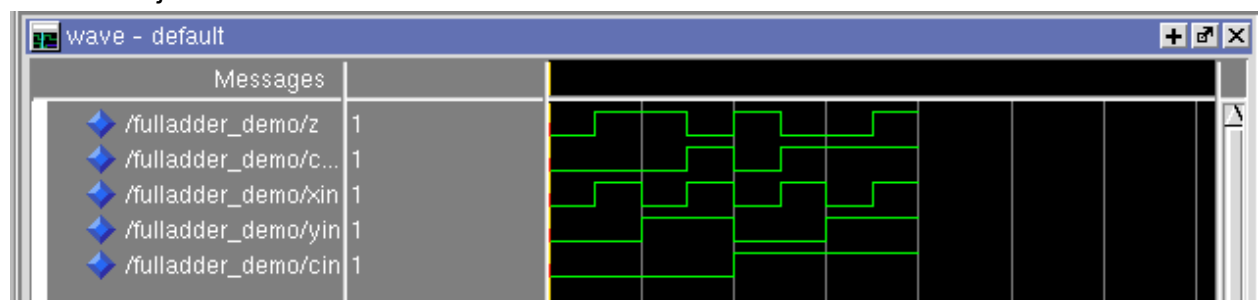6. The simulate will start and finish shortly. The zoom level might not fit the waveform. Zoom in or out to adjust the waveform.



7. The waveform is as our expectation.

### Summary of the workflows.

Here is a summary of the workflows:

1. Create a project.
2. Add and edit files, including testbenches.
3. Compile all the files.
4. Open the simulation window.

5. Add signals to wave.
6. Run the simulation and check results.

## SRAM Reader

The next demo is to give an example on how to use SRAM component provided by the library.

1. Copy the file "data/sort\_corrected\_branch.dat" in the library package to your project location.
2. Add the SRAM demo file "sram\_demo.vhd" and write the following content to it.

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

use work.eecs361_gates.all;
use work.eecs361.all;

entity sram_demo is
    port (
        dout : out std_logic_vector(31 downto 0)
    );
end sram_demo;

architecture structural of sram_demo is
    signal cs : std_logic;
    signal oe : std_logic;
    signal we : std_logic;
    signal addr : std_logic_vector(31 downto 0);
    signal din : std_logic_vector(31 downto 0);
    signal ctrl_bus : std_logic_vector(2 downto 0);
begin
    sram_map : sram
        generic map (mem_file => "sort_corrected_branch.dat")
        port map (cs => cs, oe => oe, we => we, addr => addr, din => din,
dout => dout);
    cs <= ctrl_bus(2);
    oe <= ctrl_bus(1);
    we <= ctrl_bus(0);


    process
        variable vaddr : integer range 0 to 2147483647;
    begin
        ctrl_bus <= "110";
        for vaddr in 4194336 to 4194376 loop
            addr <= std_logic_vector(to_unsigned(vaddr, 32));
            wait for 5 ns;
        end loop
    end process
end structural;
```

```

    end loop;
    wait;
end process;
end;
```

3. Start the simulation of sram\_demo with all the signals.

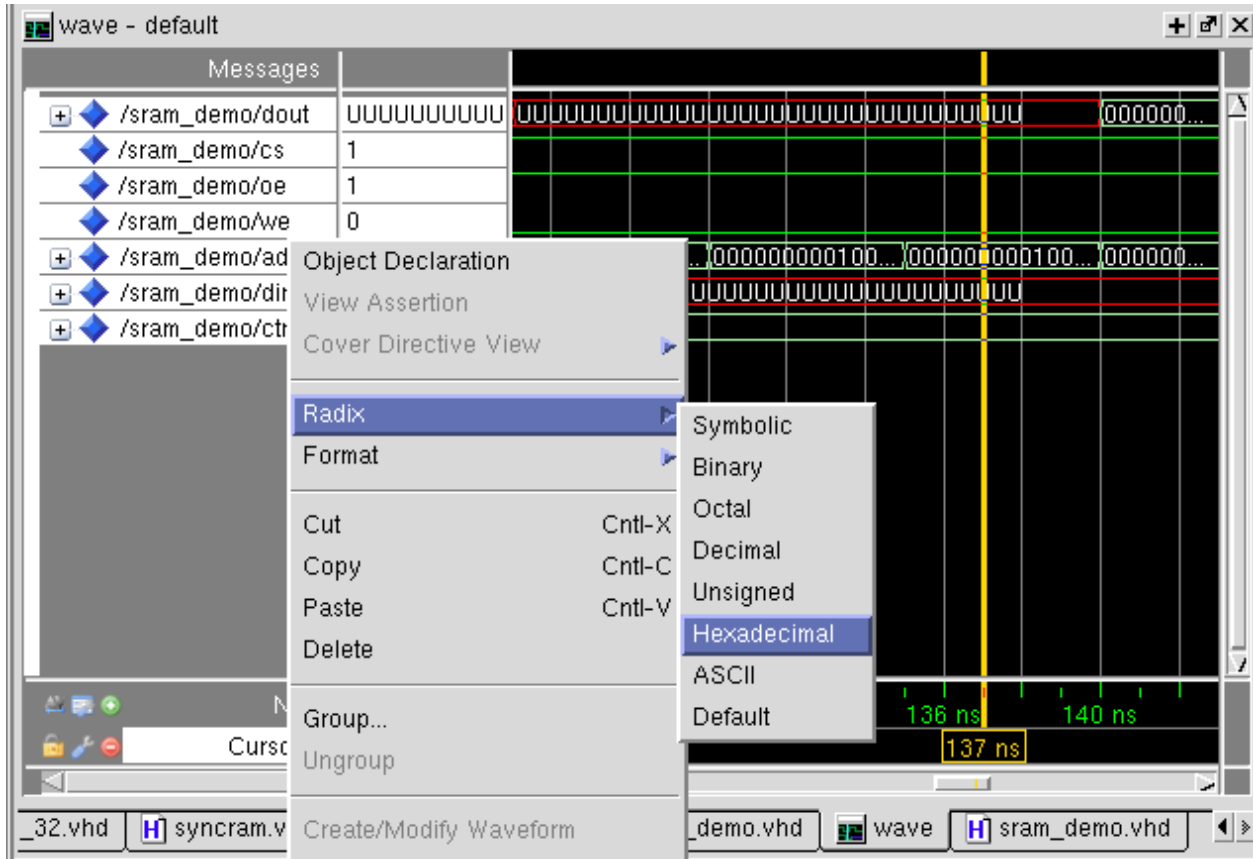4. You can change the display format of the signal. To do that, select the signals, and right click on them, then select Radix -> Hexadecimal.



5. The waveform is similar to the mentor graphics one, except the VHDL SRAM use '1' to enable the chip.

